

## Problem Solving, Hardware Style

An LED requires 2-volts to light up nice and bright. A 9-volt battery is available.  
 How many volts must be "thrown away?" \_\_\_\_\_ **V**

Follow the Lab Sheet Punch List to gather data that will be plugged into Ohm's Law.

