

NAME \_\_\_\_\_

DATE \_\_\_\_\_

An LED requires approximately 2 volts to light up. A 9-volt battery is available. How many volts must be 'thrown away' by the current limiting resistor so that the LED will not be damaged? \_\_\_\_\_ V

**step-1:** measure the disconnected battery voltage,  $V_{NL}$  and enter next to the battery.

**step-2:** determine the resistor value based on color code and enter in the box provided below.

**note:** To measure current, the 'switch' between the resistor and the LED Anode represents a place to insert the multimeter when set to the OFF position.

**step-3:** measure the resistor value with the multimeter:

**step-4:** Connect the battery, LED and Resistor.

If the LED is lit, then measure

$V_{NL} =$  \_\_\_\_\_  
NL = No Load

$V_{FL} =$  \_\_\_\_\_  
FL = Full Load

**step-5:** measure the voltage across the resistor,  $V_R$ , and enter that number above the resistor.

**step-6:** measure  $V_{LED}$  and enter above the LED.

**step-7:** Enter and prove:  $V_R$  \_\_\_\_\_ +  $V_{LED}$  \_\_\_\_\_ = \_\_\_\_\_ =  $V_{FL}$ . If not, find your mistake.


**step-7:** Use Ohm's Law to **calculate** the current THROUGH the Resistor  $V_R$  \_\_\_\_\_  $\Omega =$  \_\_\_\_\_ Amps

**step-8:** Break the circuit to measure the current with the Multimeter = \_\_\_\_\_ mA

**note:** .001 Amp = 1 mA (milli-Amp)



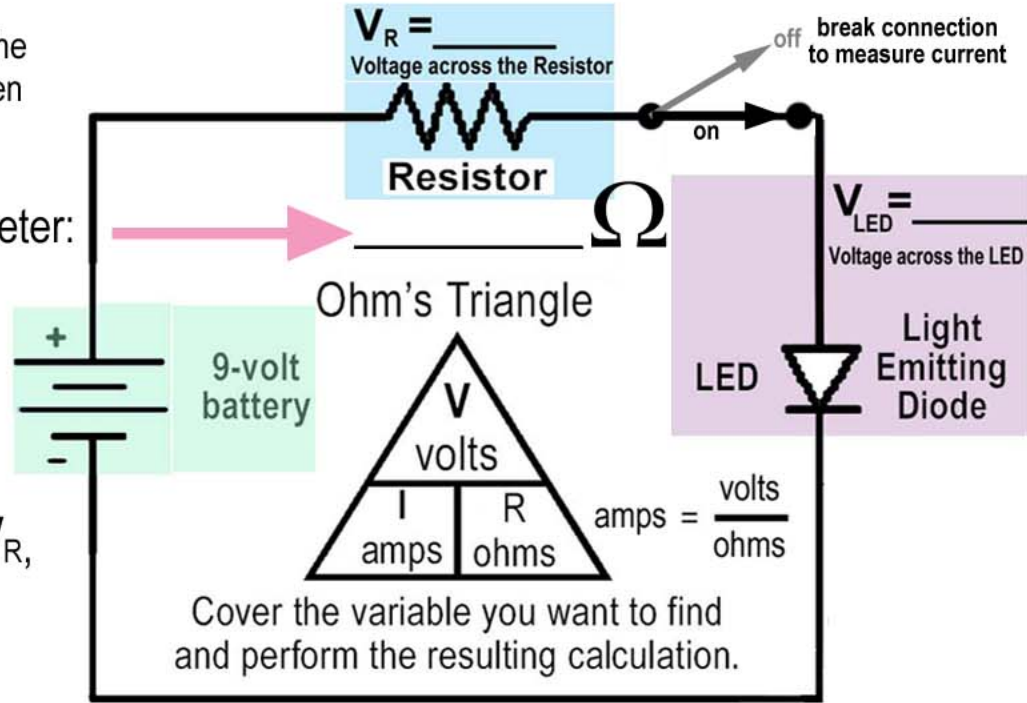DC Resistance and AC Impedance are in Ohms



1st BAND	2nd BAND	MULTIPLIER		TOLERANCE
				← colors
		X	=	$\Omega$ @ %