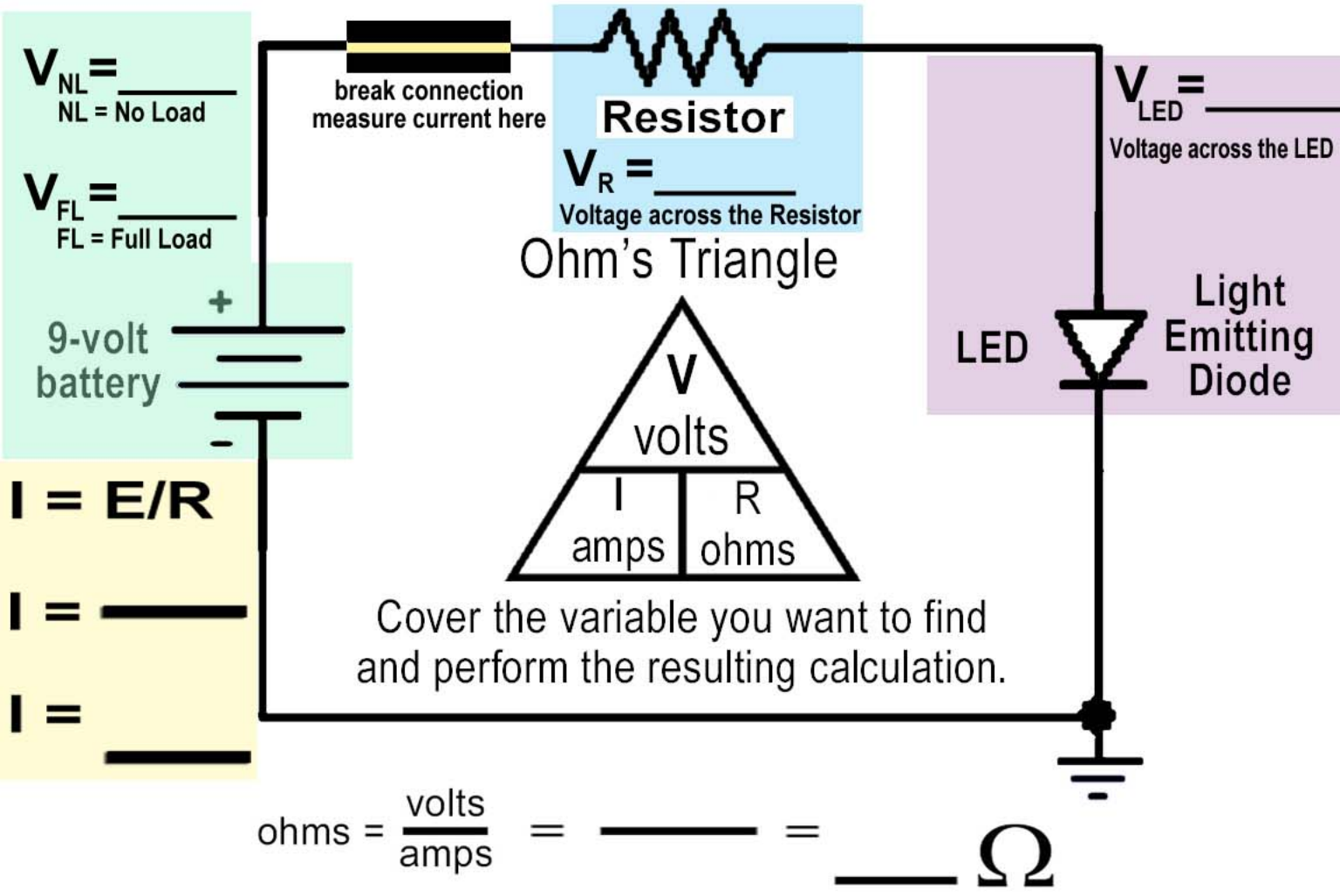


Problem Solving, Hardware Style

An LED requires 2-volts to light up nice and bright. A 9-volt battery is available. How many volts must be “thrown away?” V
 If the LED consumes 10 milli-Amperes (mA) at max brightness, calculate the resistor value using OHM’s Law... Ω



- STEP-1:** Choose the Ohm’s law variation that solves for Resistance.
- STEP-2:** Plug in the correct known quantities keeping in mind that the voltage drop *across* the resistor is needed and that the current *through* the LED is the same everywhere else in the circuit.
- STEP-3:** Does the voltage across the resistor plus the voltage across the LED equal the voltage supplied by the battery?