



NOTES:

- 1.) Add (and label) the three items that are missing on the left side of the transformer to make it functional.
- 2.) Label the two primary components in this circuit.
- 3.) What is the name of this circuit and what does it do? _____
- 4.) Place the appropriate letter and number within each half wave.
- 5.) The two components that are missing from the right side of the rectifier are _____
- 6.) Draw their effect on the half waves.

NAME: _____ DATE: _____