
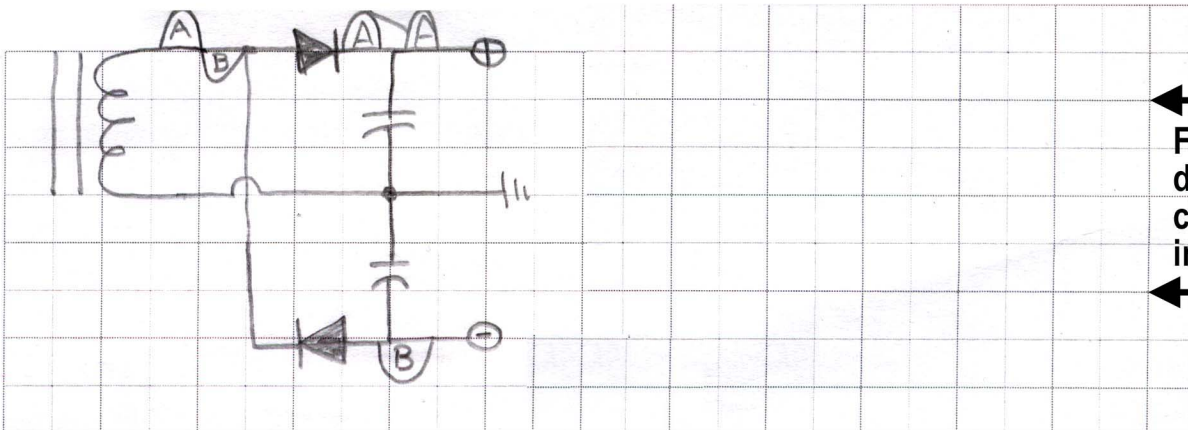
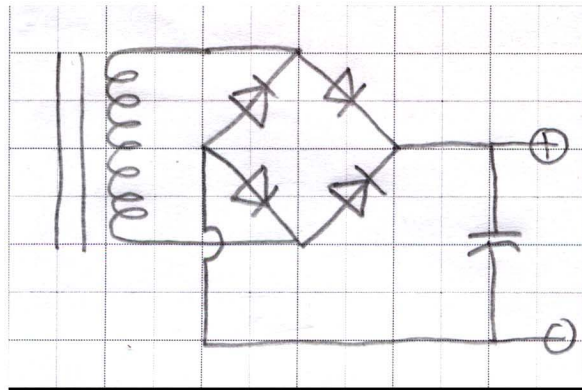
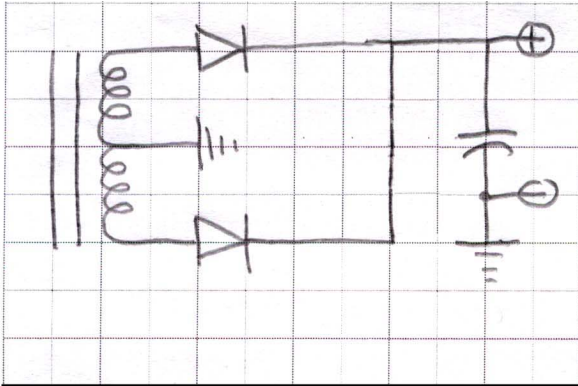


NAME THAT RECTIFIER

For each circuit, specify whether one or two voltages are made (SE or BP) and whether one half or both halves of a sine wave are rectified (HW or FW). Where applicable, also specify whether the diodes are in Full Wave (FW) or Bridge Rectifier (BR) configuration.

Name _____

Date: _____

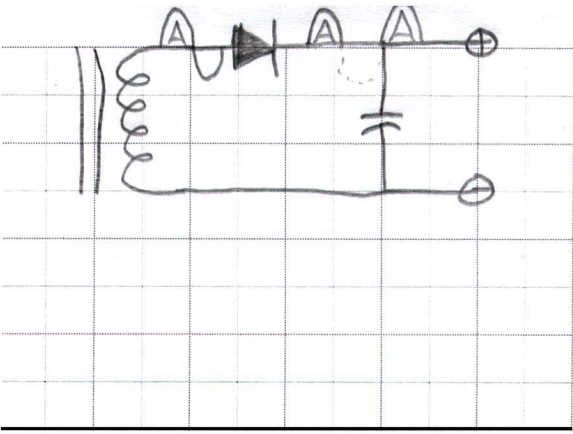


For this circuit,
draw zener shunt
clamps, plus
indicator LEDs

What Belongs Here? (draw)

power, fuse and switch



What Belongs Here? (draw)

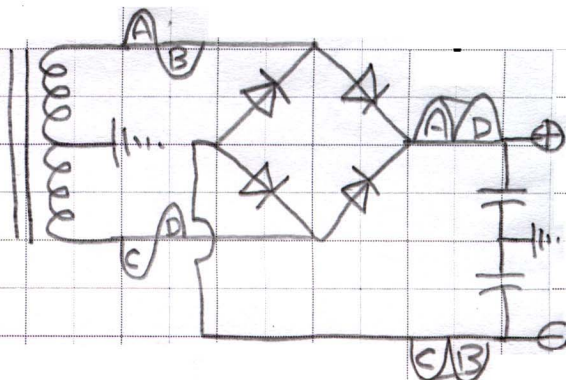

(think 3-terminal device, use generic "xx" part number or specific "ADJ" part #)

