





NAME THAT RECTIFIER

(type and voltage(s) produced...)

“SE” or “BP,” “HW” or “FW,” “BR” or “VD”)

Name _____

Date: _____

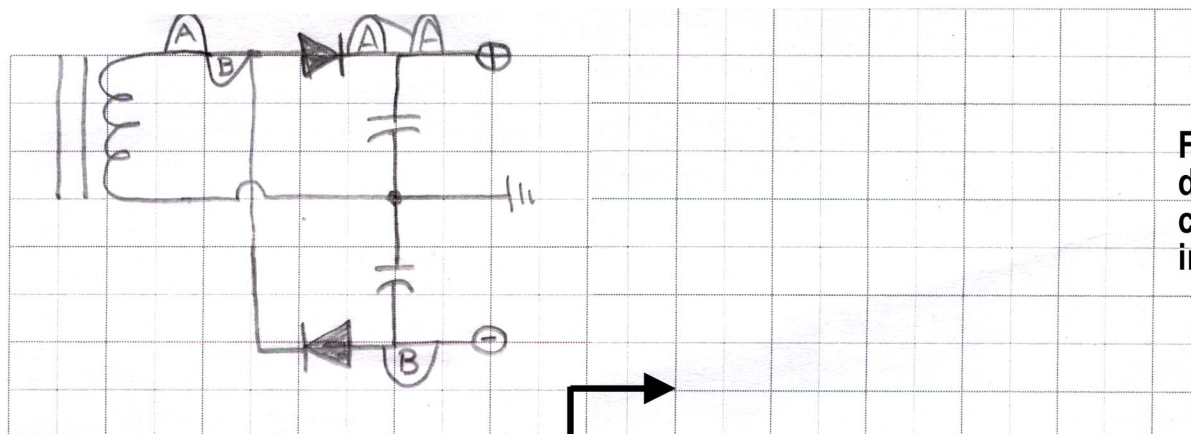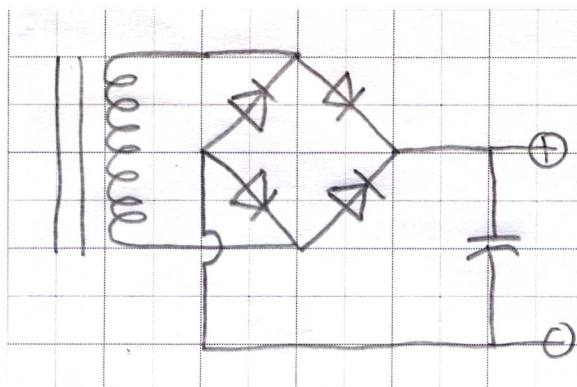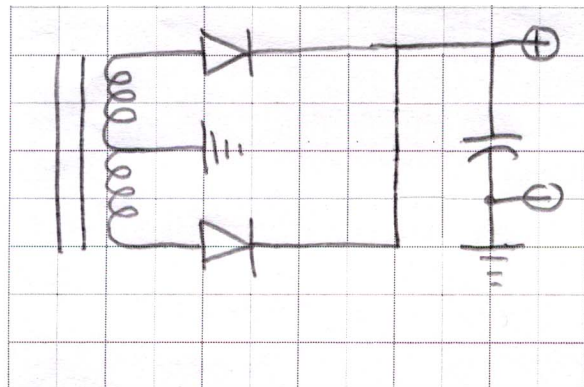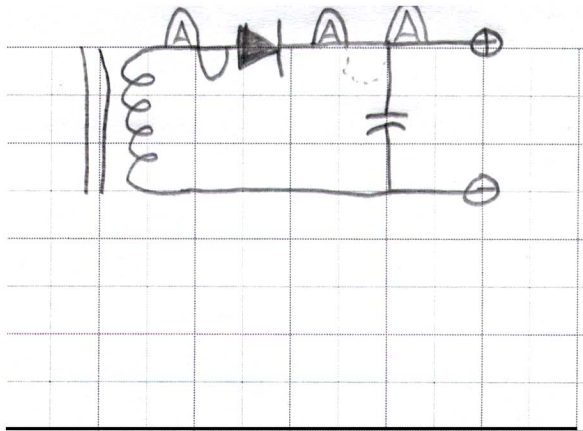


For this circuit, draw zener shunt clamps, plus indicator LEDs

name of these circuits and what they make

What Belongs Here? (draw)

What Belongs Here? (draw)

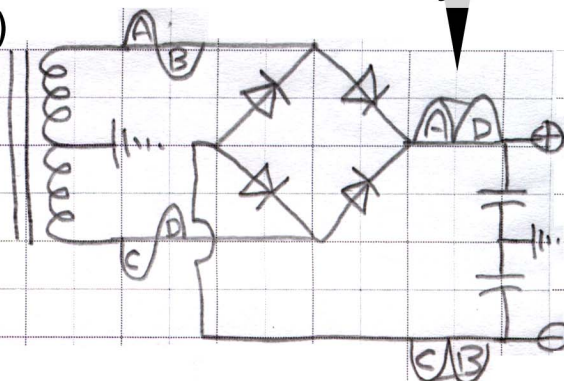

(think 3-terminal device, use generic “xx” part number or specific “ADJ” part #)

