

by Scott Hampton

sound. The tube circuit has more headroom, and a bigger presence in the bottom end, but the JFET amp is very clean in the upper end, and has a very flat and tight low end. I actually like it better than the tube circuit as a bass DI (if forced to go direct). With the proper gain structure on the front end, the JFET amplifier can deliver a very accurate and musical sound. The fun starts when you overdrive the shit out of it. The distortion characteristics of the JFET based mic preamp are just as useful (if not more) than its merit as a clean and accurate mic preamp. And jumpering one JFET mic preamp into another, and working the two pads and volume controls, unleashes a palette of sonic evil.

The figure contains two circuit diagrams. The left diagram is for an N Channel JFET amplifier. It features an input terminal connected to the gate of the JFET through a 1-10M resistor. The source is connected to ground through a parallel combination of a 470uF capacitor and a 1.8k resistor. The drain is connected to a +24VDC supply through a 15k resistor and to the output terminal through a 10uF capacitor. The right diagram is for a Triode (Tube) amplifier. It features an input terminal connected to the grid of the tube through a 1-10M resistor. The cathode is connected to ground through a parallel combination of a 470uF capacitor and a 2K resistor. The plate is connected to a +250VDC supply through a 100K resistor and to the output terminal through a 1uF capacitor. A Vf symbol is shown near the cathode.

(amplified and inverted in phase). A 50-ohm resistor has been added that is not bypassed by the 470 μ f cap, which reduces the third harmonic by about 20dB. The NPN transistors act as a voltage follower providing the output drive, with near unity gain. The dc voltage on the drain is slightly above the supply, and directly biases the MPSA14 Darlington transistor. A Darlington is used to minimize the loading on the 2N5457 (Darlington transistors have a much higher input impedance). The ZTX653 is a generic NPN transistor acting as an active load ($\beta = 100$ min). Since the output also has roughly 1/2 the supply voltage on it, a coupling capacitor on the output is required to block the DC but allow the audio signal to pass. This is a key component and worth a few extra bucks for a good quality polypropylene capacitor or better.

FIG 2

Q = 1/4W
H = 1/2W
1% METAL FILM

There are as many ways to buffer a signal as there are signals, so I leave it up to the reader to explore more esoteric designs if desired. The one shown here works great, and in my opinion is not compromised in any way just because of its simplicity. This circuit (figure 2) will from here on be referred to as the JFP (JFET preamp) and represented by the purple triangle. The input impedance of the JFP is basically the value of resistance on the gate to ground, and can be as high as 1000Mohms. The gain is approximately +26 dB, with the signal at the output being out of phase with the input.

FIG 3

MICROPHONE PREAMPLIFIER

The diagram illustrates a microphone preamplifier circuit with the following components and connections:

- Input Section:** Includes an 'INST INPUT' and a switch 'T' leading to a transformer 'TX'. The 'MIC INPUT' section features a transformer 'TX 1:10' and a 48VDC phantom power supply (470uF 63V, 6.8K X2, 470H).
- First Amplifier Stage:** A JFET amplifier (JFP) with a 10M resistor and a 470uF 63V capacitor. It is biased with a +24VDC supply (33H, 33H, 470uF 63V).
- Second Amplifier Stage:** Another JFET amplifier (JFP) with a 5-10k AT resistor and a 470uF 63V capacitor, also biased with +24VDC.
- Output Section:** The signal is coupled to a transformer 'TX 1:1' and a switch for 'LINE OUTPUT'.
- Voltage Regulation:** A separate section shows an LM7824 voltage regulator providing a +24VDC supply from a 'WALLWART' source (28-35VDC input). The regulator is biased with 470uF 63V capacitors and includes a 1N4007 diode.

FIG 4

LINE LEVEL MIXER: Figure 5 shows an N into 1 mixer, where N is the number of inputs. Each line input goes directly into a 10 K AT (audio taper) pot. The output of each pot goes through a 150 K resistor then connects together to form a summing node. The loss of the summing network increases the more channels you add; the overall gain with the JFP is shown. Since the JFP gain stage is inverting, the output transformer is wired out of phase, so the input and output are in phase. A 600:600 ohm transformer can be added to each input if balanced inputs are required. If more channels are desired or more overall gain, an additional JFP stage is needed. In this case, wire the summing node directly to the input of the first JFP stage, and the master volume between the two JFP stages just like in the mic preamp (figure 4). It is important for noise reasons to keep the summing resistors as close to the JFP input as possible, and shield this circuit from noise sources.

I built a two channel version of this with transformers on both the input and output, run from a 24 VDC 500 mA wall wart (shown in photo). Most unregulated power supplies output voltage is rated at a given load current. If you draw less than the rated value, the voltage will tend to be higher. The 24 VDC wall wart I used actually puts out almost 31VDC under the load of two mic preamp channels (approximately 165 mA). Because there is extra voltage, a LM7824 linear regulator was added to clean up the power. The regulator requires only 3 external parts, and an input of +28 VDC to 35 VDC to regulate properly. To decouple the two stages and filter the power further, a 33 ohm resistor and 470 μ f cap LP filter was added to each JFP gain stage.

FIG 5

N CHANS	GAIN dB
4	+11
6	+8
8	+6
12	+3
16	+1

Scott@Hamptone.com